

## QUIZ 1

NAME

DATE

CLASS PERIOD

1. Draw the electronic symbol of a resistor.



2. Draw the electronic symbol of a potentiometer used as a variable resistor.



3. In a series circuit, what effect does increasing the resistance have on the current?

**In a series circuit, current and resistance are inversely related. Therefore, the current will decrease as the resistance of the circuit is increased.**

4. What units are used to express resistance?

**Ohms ( $\Omega$ )**


5. Convert the following resistor values to Ohms.

**1.2 k $\Omega$     1200  $\Omega$**

**0.68 k $\Omega$     680  $\Omega$**

**47 k $\Omega$     47000  $\Omega$**

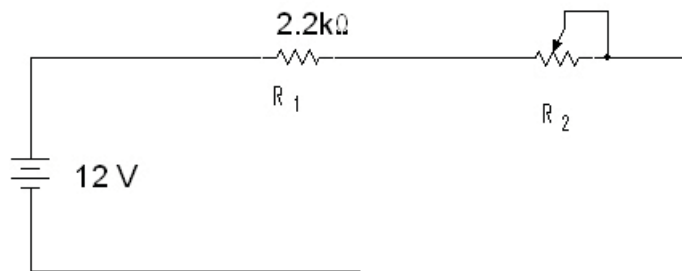Questions 6-10 relate to the circuit shown.



6. Calculate the circuit current if  $R_2$  is set to 3.3 k $\Omega$ .

$$\mathbf{R_T = R_1 + R_2 = 2200 \Omega + 3300 \Omega = 5500 \Omega}$$

$$\mathbf{V = I * R_T}$$

$$\mathbf{I = V / R_T}$$

$$\mathbf{I = 12 / 5500 = .00218 A}$$

## QUIZ 1

NAME

DATE

CLASS PERIOD

7. With  $R_2$  set to 3.3 kW, calculate the voltage drop across  $R_1$  and  $R_2$ .

**Across  $R_1$ :  $V_1 = I * R_1$**

$$V_1 = .00218 * 2200$$

$$V_1 = 4.8 \text{ V}$$

**Across  $R_2$ :  $V_2 = I * R_2$**

$$V_2 = .00218 * 3300$$

$$V_2 = 7.2 \text{ V}$$

8. If the voltage drop across  $R_1$  is measured to be 6V, what is the value of  $R_2$  in kW?

**$V_1 = 6 \text{ Volts} = I * R_1$**

$$I = 6 / R_1$$

$$I = 6 / 2200$$

$$I = .0027 \text{ A}$$

$$V_1 + V_2 = V_T$$

$$6 + V_2 = 12$$

$$V_2 = 6 \text{ Volts}$$

**$V_2 = 6 \text{ Volts} = I * R_2$**

$$R_2 = 6 / I$$

$$R_2 = 6 / .0027$$

$$R_2 = 2200 \Omega$$

$$R_2 = 2.2 \text{ k}\Omega$$

9. What is the maximum possible resistance in the circuit and what would the corresponding current be?

**(PLEASE NOTE: WE FOUND THIS QUESTION AMBIGUOUS, AND RECOMMEND YOU DISREGARD ANY ANSWERS GIVEN)**

10. If  $R_2$  is set to 5 kW, what voltage is measured across  $R_1$ ?

$$R_T = R_1 + R_2 = 2200 \Omega + 5000 \Omega = 7200 \Omega$$

$$V_T = I * R_T$$

$$I = V_T / R_T = 12 / 7200 = .00166 \text{ A}$$

$$V_1 = I * R_1 = .00166 * 2200 = 3.667 \text{ Volts}$$