

QUIZ 2

NAME

DATE





CLASS PERIOD

Put a check in the ☐ next to the correct answer.

1. What is a resistor?

- ☐ voltage source
- ☐ an electronic component that enhances current flow
- ☒ an electronic component that opposes current flow
- ☐ an electronic component that is rarely used in electronic circuits

2. What is the electronic symbol of a resistor?

- ☐ 
- ☐ 
- ☐ 
- ☒ 

3. Increasing the _____ in an electronic circuit causes a drop in the amount of current.

- ☐ source voltage
- ☒ resistance

4. What units are used to express resistance?

- ☐ farads
- ☐ volts
- ☒ ohms
- ☐ amperes

5. Convert each of the following resistor values to Ohms:

a. $R = 2 \text{ kW}$

i. 200 W

ii. 2 W

iii. 2000 W

iv. .002 W

b. $R = 6.8 \text{ kW}$

i. 680 W

ii. .068 W

iii. 6800 W

QUIZ 2

NAME

DATE

CLASS PERIOD

6. What is a potentiometer?

- ☐ An electronic component that is basically used as a variable resistor or as a voltage divider
- ☐ an electronic device that is used to measure the potential difference between two points on a circuit
- ☐ an electronic device that is used to measure resistance

7. In a series electronic circuit with $E = 12V$, $R_1 = 4\text{ kW}$, $R_2 = 5\text{ kW}$, the current is equal to:

- ☐ 3 A
- ☐ 3 mA
- ☐ 1.333 mA
- ☐ 2.4 mA

8. For the same circuit in question 7, the voltage drop across R_2 is:

- ☐ 15 V
- ☐ 6.667 V
- ☐ 12 V

9. In a series circuit with $E = 10V$, $R_1 = 2\text{ kW}$, and the voltage drop across R_2 is 7.5 volts. The voltage drop across R_1 is:

- ☐ 7.5 V
- ☐ 2.5 V
- ☐ 10 V
- ☐ 0 V

10. For the same circuit in question 9, the value of R_2 is:

- ☐ 7.5 kW
- ☐ 6 kW
- ☐ 2 kW
- ☐ 10 kW