

**QUIZ** / How much current will my robot draw?

NAME \_\_\_\_\_

DATE \_\_\_\_\_

CLASS PERIOD \_\_\_\_\_

**Put a check ✓ in the  next to the correct answer.**

$$V = I \times R$$

1. What is current?
  - A movement of volts
  - The flow of electric charge
  - The splitting of electrons
  - The electromotive force (pressure) of electricity
2. What is the voltage of a circuit with a resistance of 1000 ohms and a current of 0.16 amps? Use the formulas at left.
  - 6250 V
  - 0.00016 V
  - 160 V
3. What is the resistance of a circuit with a voltage of 1.5 V and a current of 0.16 amps? Use the formulas at left.
  - 0.24 ohms
  - 0.106667 ohms
  - 9.375 ohms
4. A battery produces:
  - Alternating current
  - Direct current
5. You have attached four AA (1.5 V) batteries together in series. If you use your multimeter to measure the voltage of this circuit, what do you expect the reading to be?
  - 6 V
  - 1.5 V
  - 0.375 V
6. If your robot does 0.5 J of work for 10 milliseconds, how much power does it produce? Use the formulas at left.
  - 5 Watts
  - 0.005 Watts
  - 50 Watts
7. If your robot is powered by a 7.2 V battery and produces 2.16 W of power, how much current is your robot drawing? Use the formulas at left.
  - 3.33 A
  - 0.3 A
  - 15.552 A
8. Your robot is powered by two 1.5 V batteries in series. If your robot is drawing 0.1 amps of current for 10 s, how much work does your robot do? Use the formulas at left.
  - 3 J
  - 0.03 J
  - 1.5 J
9. What will happen if a 12 volt battery is used on a 6 volt motor?
  - Destroy the motor
  - Make the motor run very slow
  - The motor will not run

$$Work_1 = F \times d$$

$$Work_2 = V \times I \times t$$

$$Power_1 = \frac{W}{t}$$

$$Power_2 = V \times I$$

**QUIZ** / How much current will my robot draw?

NAME

DATE

CLASS PERIOD

- 10.** The amount of work done by your robot in this lab is directly proportional to:  
(check all that apply)
- The friction of the ramp
  - Current draw of the robot
  - The battery voltage of the robot
  - The number of seconds it takes the robot to go up the ramp
  - The total resistance of the robot
- 11.** What will happen to the current draw on the motor if the incline is increased from  $5^\circ$  to  $30^\circ$ ?
- Remain the same       Decrease       Increase
- 12.** What symbol setting should the multimeter be on to measure direct current?
- $\bar{A}$                         $\bar{I}$                         $\bar{A}$
- 13.** What will happen to the current reading when the drive gear is much larger than the driven gear?
- Current reading will stay the same
  - Current reading will increase
  - Current reading will decrease
- 14.** List one factor that affects the current drawn in your motor. Explain why this factor affects current.